


Lab 5: Character LCD Control



National Chiao Tung University
Chun-Jen Tsai
10/17/2017

Lab 5: Character LCD Control

 - ❑ In this lab, you will use the sieve algorithm to find all the primes from 2 to 1021, and use the standard 1602 character LCD to display the prime numbers



- ❑ The deadline of the lab is on 10/24

1602 Character LCD Display

- ❑ The Arty board has only simple I/O devices such as LEDs, switches, buttons, and UART
- ❑ We have designed an expansion board, Arty_IO, that adds three more peripherals to Arty:
 - 1602 character LCD devices (supports only 4-bit mode)
 - SD card socket (supports only the SPIF mode)
 - 12-bit color VGA interface

Memory Map of the LCD

- ❑ The LCD device can be treated as a 32-byte memory
 - Each memory cell corresponds to a character on the display
 - Writing an ASCII code to a cell will display the character on the corresponding location on the LCD:



Note: the LCD device is slow, you should not update the screen faster than 2 Hz.

- ❑ Display data memory (DD RAM) addresses:

1	00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F
2	40	41	42	43	44	45	46	47	48	49	4A	4B	4C	4D	4E	4F
	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16


Character LCD Interface (1/2)

- ❑ The LCD interface has 8 data wires (DB0 ~ DB7) and 3 control wires (LCD_E, LCD_RS, LCD_RW):
 - LCD_E enable/disable the inputs to the LCD module
 - The rest of the wires are defined depending on the functions:

Function	LCD_RS	LCD_RW	Upper Nibble				Lower Nibble			
			DB7	DB6	DB5	DB4	DB3	DB2	DB1	DB0
Clear Display	0	0	0	0	0	0	0	0	0	1
Return Cursor Home	0	0	0	0	0	0	0	0	1	-
Entry Mode Set	0	0	0	0	0	0	0	1	I/D	S
Display On/Off	0	0	0	0	0	0	1	D	C	B
Cursor and Display Shift	0	0	0	0	0	1	S/C	R/L	-	-
Function Set	0	0	0	0	1	0	1	0	-	-
Set CG RAM Address	0	0	0	1	A5	A4	A3	A2	A1	A0
Set DD RAM Address	0	0	1	A6	A5	A4	A3	A2	A1	A0
Read Busy Flag and Address	0	1	BF	A6	A5	A4	A3	A2	A1	A0
Write Data to CG RAM or DD RAM	1	0	D7	D6	D5	D4	D3	D2	D1	D0
Read Data from CG RAM or DD RAM	1	1	D7	D6	D5	D4	D3	D2	D1	D0


Character LCD Interface (2/2)

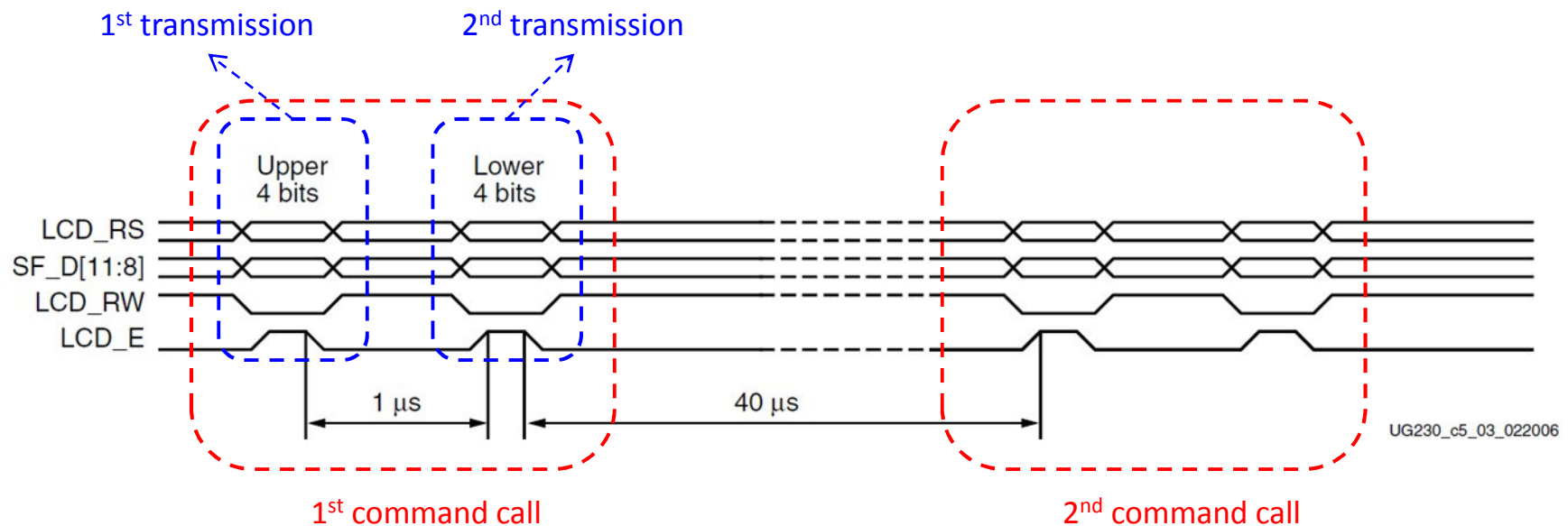- ❑ However, the Arty_IO board uses the 4-bit operating mode of the LCD device, that is, only DB4~DB7 are connected to the FPGA
 - Execution of a function will need two transmissions, using only LCD_E, LCD_RS, LCD_RW, and DB4~DB7:





Timing Diagrams for Transmission

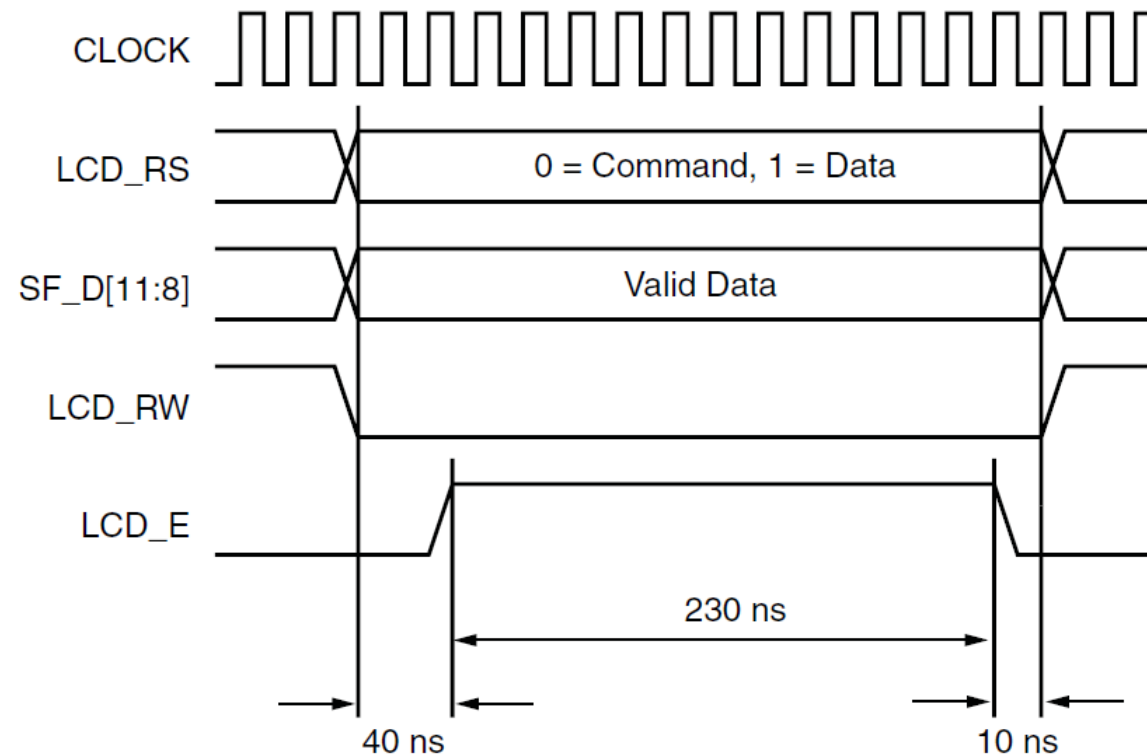- ❑ The timing diagram for one transmission in four-bit mode is as follows:
 - Note that execution of a function requires two transmissions



The Sample Circuit of Lab5

- ❑ Two Verilog program files will be provided to you:
 - LCD_Module.v – An LCD controller module
 - Lab5.v – a sample top-level module that prints a “Hello, World!” message using the LCD controller module

```
module LCD_module(  
    input clk,  
    input reset,  
    input [127:0] row_A,  top-row of text  
    input [127:0] row_B,  bottom-row of text  
    output reg LCD_E,  
    output reg LCD_RS,    //register select  
    output reg LCD_RW,    //read / write  
    output reg [3:0] LCD_D //data  
);
```


The Sieve Algorithm (1/2)

- ❑ The sieve algorithm is an interesting algorithm to find prime numbers using only addition operations:

```
#define LIMIT 1024

unsigned char primes[LIMIT];

memset((void *) primes, 1, sizeof(primes));

/* sieve algorithm */
for (idx = 2; idx < LIMIT; idx++)
{
    if (primes[idx])
    {
        for (jdx = idx+idx; jdx < LIMIT; jdx += idx)
        {
            primes[jdx] = 0;
        }
    }
}
```

→ Turn these nested loops into a circuit!

The Sieve Algorithm (2/2)

- ❑ After running the Sieve algorithm, the array `primes[]` contains flags of whether a number is a prime or not
 - `primes[n] == 1` means `n` is a prime number,
`primes[n] == 0` means `n` is not a prime number
- ❑ In your circuit, you can declare the array `primes[]` as a bit array of registers:

```
reg [0:1023] primes;
```

What to Do in Lab 5

- ❑ In Lab 5, it is **mandatory** to do the following things:
 - Design a circuit to implement the sieve algorithm
 - Once all primes between 0 and 1023 are found, the LCD will start to display prime numbers in the following format
 - Roughly every 0.7 sec, the LCD scrolls up one number cyclically
 - If BTN3 is pressed, the scrolling direction will be reversed (scroll-up becomes scroll-down, and vice versa)
 - Example display: cyclic scroll-up (**numbers are hexadecimal**)

