

Lab1: Introduction to the EDA Tools



National Chiao Tung University
Chun-Jen Tsai
9/15/2017

Lab 1 Goal: Design an 8-bit Multiplier

- ❑ In this lab, you must design an 8-bit sequential binary multiplier and use the Vivado Simulator to verify your design
 - You should review your old textbook on Digital Circuit Design by Mano. Some design guideline of the sequential binary multiplier is in section 8.7 of Mano's book.
 - You must design your multiplier using only adder, shifter, multiplexor, and gate-level operators. You can not use the multiplication operator of Verilog.
- ❑ You must demo to your TA during the Lab hours on 9/19 that your circuit works

The Target Technology of Digital Labs

- ❑ Digital circuits can be implemented in different ways
 - Circuits Boards
 - Circuit board design using standard IC parts (e.g., 74SLxx)
 - Application Specific ICs
 - Full-custom and Cell-based IC designs
 - Programmable logics
 - Field Programmable Gate Array (FPGA) design
- ❑ Here, we use Xilinx FPGAs for circuit implementation
 - Xilinx is the largest FPGA manufacturing company in the world
 - Ross Freeman, the co-founder of Xilinx, invented the very first FPGA in 1986[†]

[†] US Patent 4,870,302

Xilinx Vivado Design Suite

- ❑ Xilinx has two different EDA tools for FPGA-based digital system designs
 - Vivado Design Suite
 - Only for 7th-generation FPGAs and above
 - Unified IDE for both “SoC” and “digital circuit” designs
 - ISE Design Suite
 - For 7th- and older generations of FPGAs
 - ISE EDK for SoC designs
 - ISE Project Navigator for digital circuit designs
- ❑ In this course, we use the Vivado Design Suite for digital circuit design

Vivado Circuit Implementation Flow

- ❑ Step 1: Design Entry
 - Input your circuit design using Hardware Description Language (HDL), such as Verilog or VHDL
- ❑ Step 2: Synthesis
 - Convert from the HDL programs or schematics to a netlist file that define a list of circuit blocks and how they are connected
- ❑ Step 3: Mapping
 - Determine what FPGA resource will be used to implement which part of the netlist
- ❑ Step 4: Place-and-Route
 - Determine physical location and routing of the circuit resource
 - A “*.bit” file will be generated for the FPGA device

Vivado Circuit Debug Flow

- ❑ Your design may not be perfect in the first try!
 - Circuit debugging is done via “simulation” or “signal probing”
- ❑ Vivado supports several simulation types. In particular:
 - Behavioral simulation
 - Functional simulation before synthesis; assumes zero delay
 - Post implementation functional simulation
 - Functional simulation after synthesis; assumes zero delay
 - Post implementation timing simulation
 - Simulate signal switching of your circuit with exact signal delays on the target devices
 - Also called “post-sim”
- ❑ Vivado Logic Analyzer can analyze runtime signals

Install Your Own Vivado Design Suite

- ❑ Install a copy of Vivado Design Suite – HLx Editions 2017.2 onto your computer.

- You can download it from:


<https://www.xilinx.com/support/download.html>

- ❑ The installation requires at least 25.3 GiB of disk space
 - Please install the “WebPACK” version and register online for a free license

ISE Installation Note

- ❑ You must select the right version upon installation:

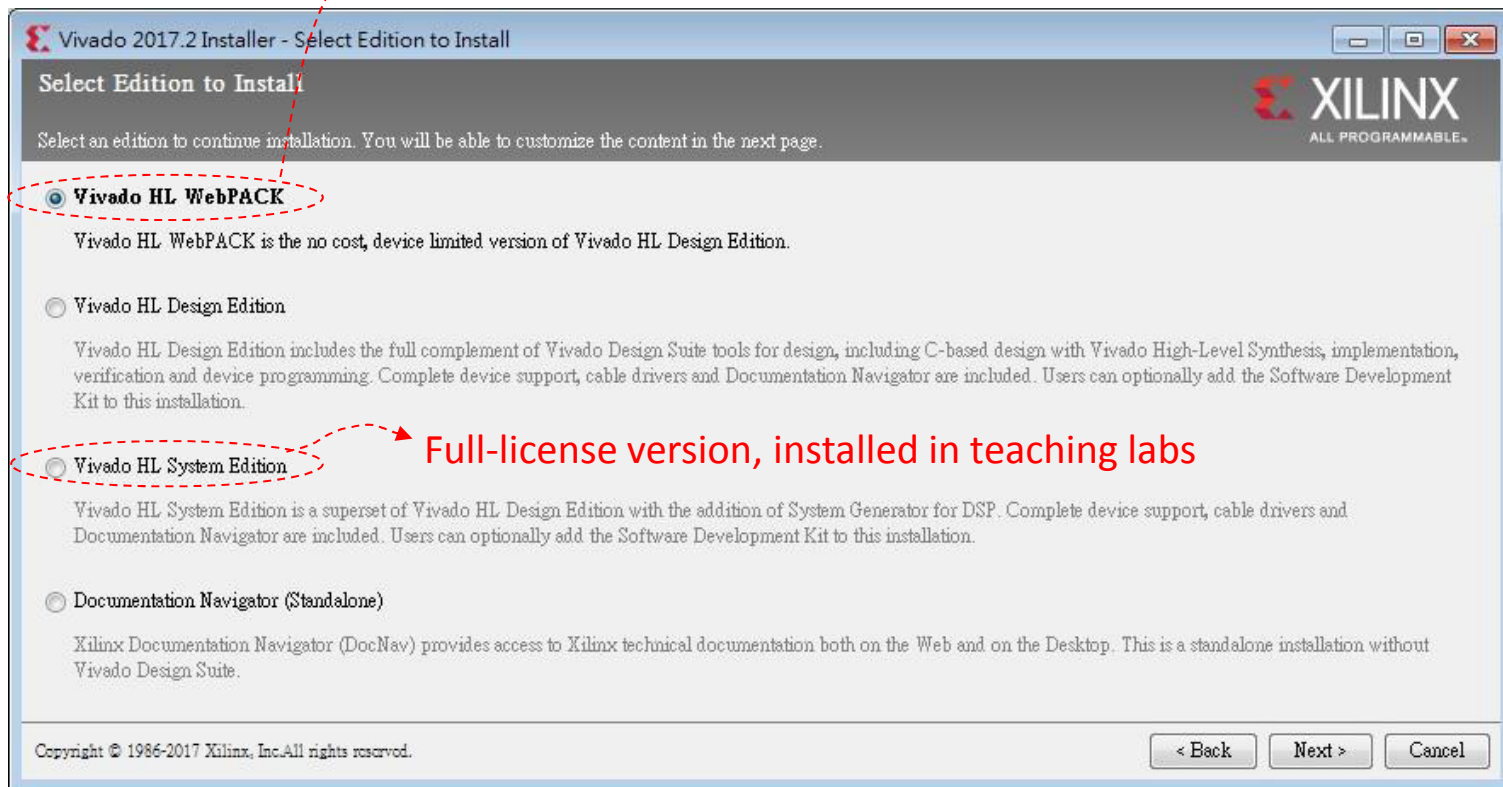
Free license version, for personal use, no Vivado Logic Analyzer



Installation of Arty Board Definitions


- ❑ After the installation of Vivado, you must install the board definition file of Arty:
 - Download arty.zip from E3.
 - Unzip arty.zip to the following directory:

 C:\<INST_DIR>\Xilinx\Vivado\2017.2\data\boards\board_files




Invoke Vivado 2017.2

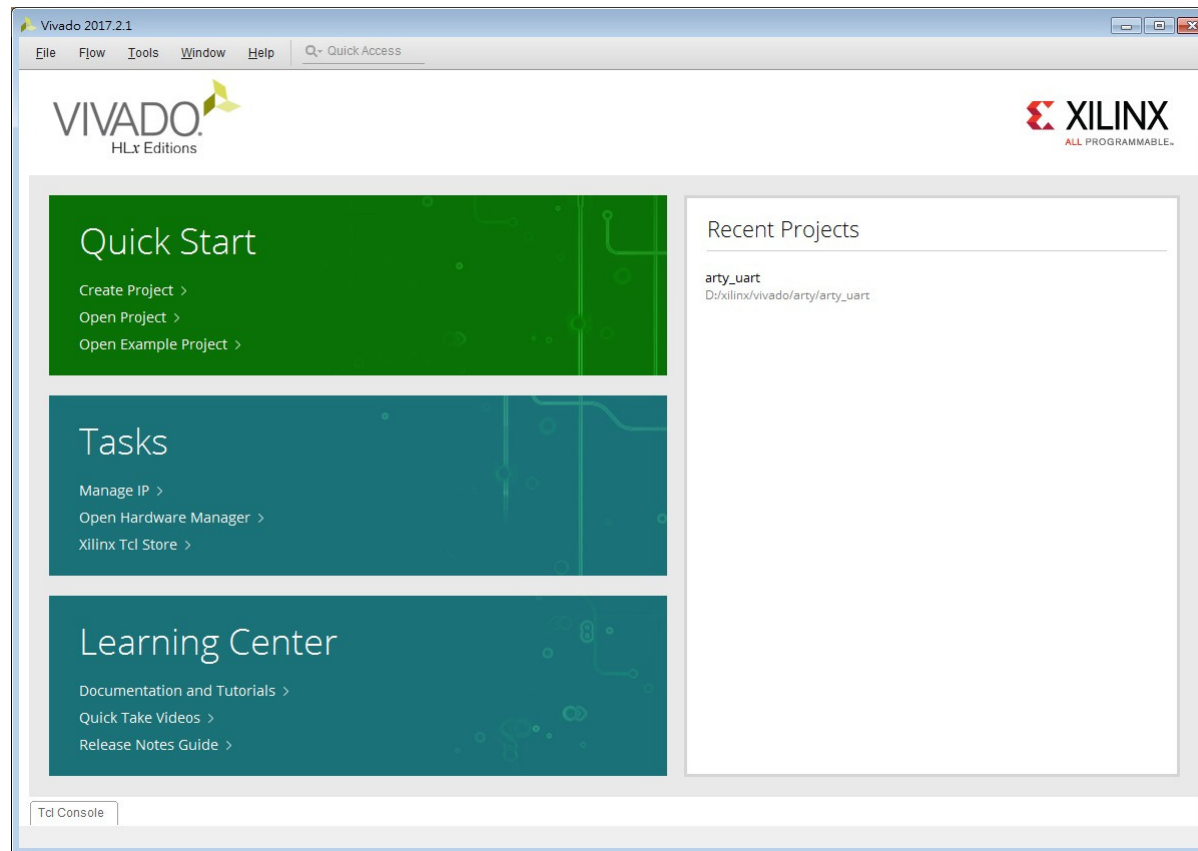
- ❑ Double-clicking the Vivado 2017.2 icon on desktop:



Create a New Project in Vivado

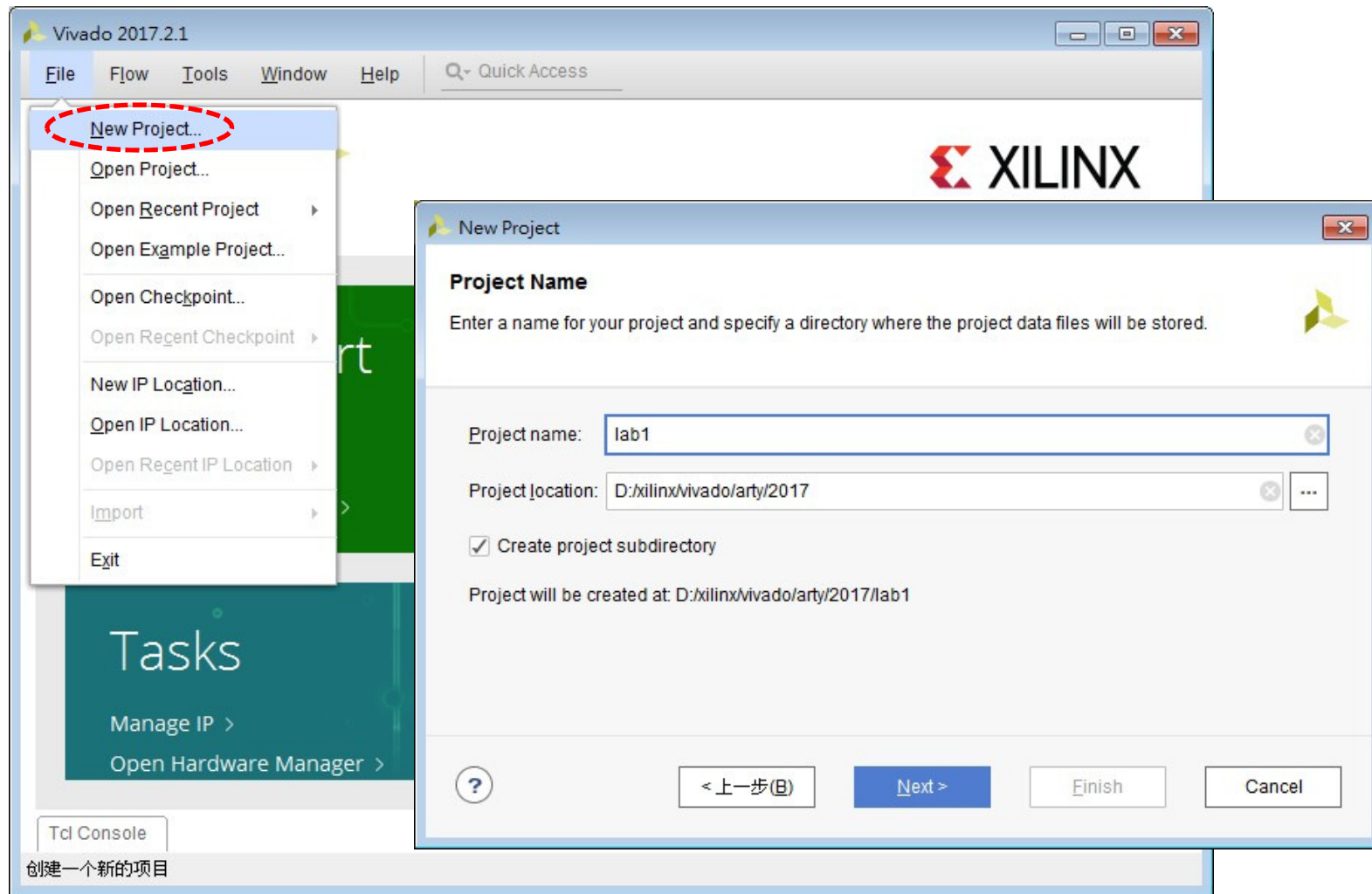

Select HDL or Schematic Design

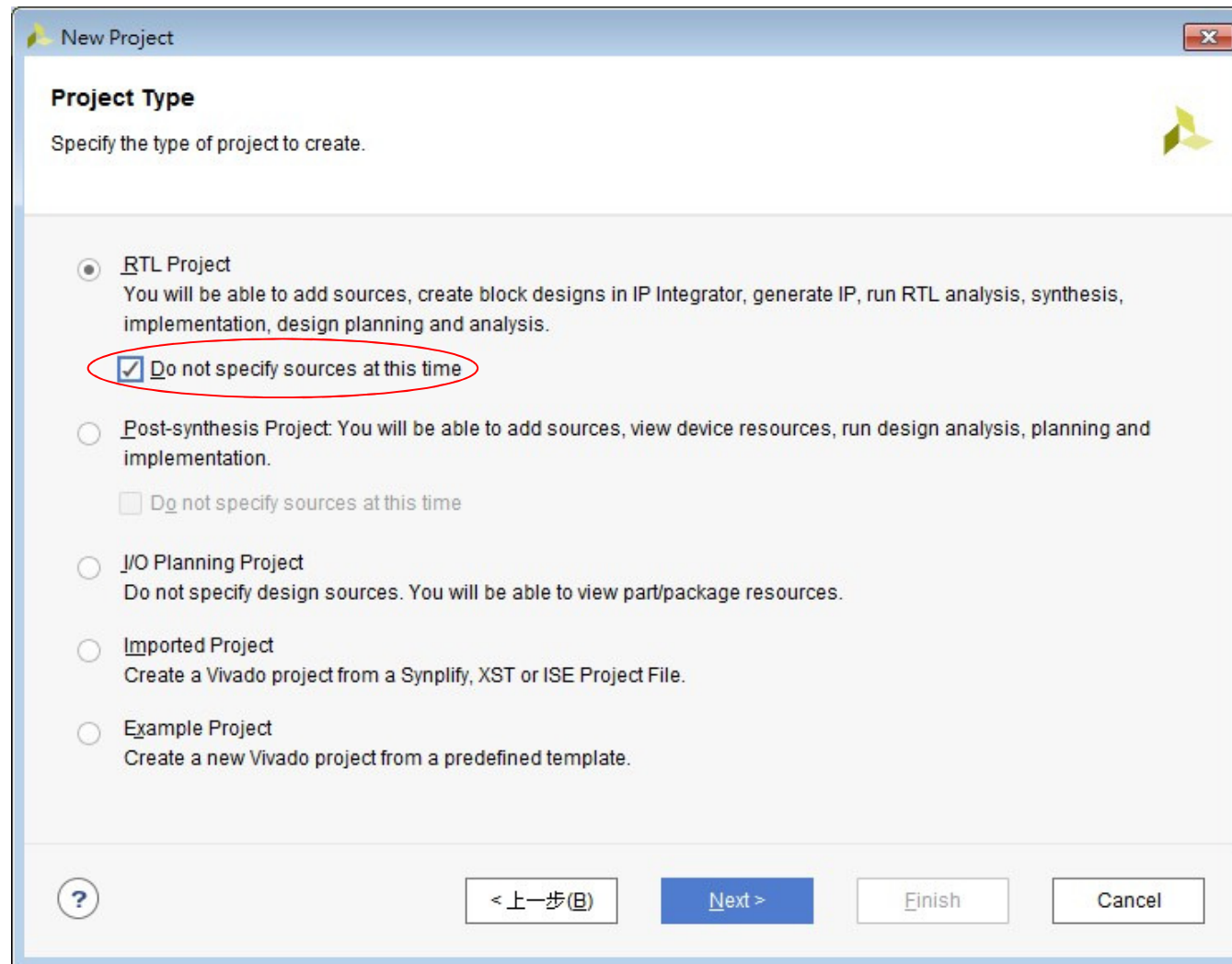

New Project

Project Type
Specify the type of project to create.

- ☒ **RTL Project**
You will be able to add sources, create block designs in IP Integrator, generate IP, run RTL analysis, synthesis, implementation, design planning and analysis.
☒ **Do not specify sources at this time**
- ☐ **Post-synthesis Project** You will be able to add sources, view device resources, run design analysis, planning and implementation.
☐ **Do not specify sources at this time**
- ☐ **I/O Planning Project**
Do not specify design sources. You will be able to view part/package resources.
- ☐ **Imported Project**
Create a Vivado project from a Synplify, XST or ISE Project File.
- ☐ **Example Project**
Create a new Vivado project from a predefined template.

? < 上一步(B) Next > Finish Cancel

Select the Target Device

New Project

Default Part
Choose a default Xilinx part or board for your project. This can be changed later.

Select: ☐ Parts ☒ **Boards**

Filter/Preview

Vendor:

Display Name:

Board Rev:


Search:

Display Name	Vendor	Board Rev	Part	I/O Pin C
Arty	digilentinc.com	C.0	xc7a35ticsg324-1L	324

< >


No Board Connectors

Add a New HDL Source Code

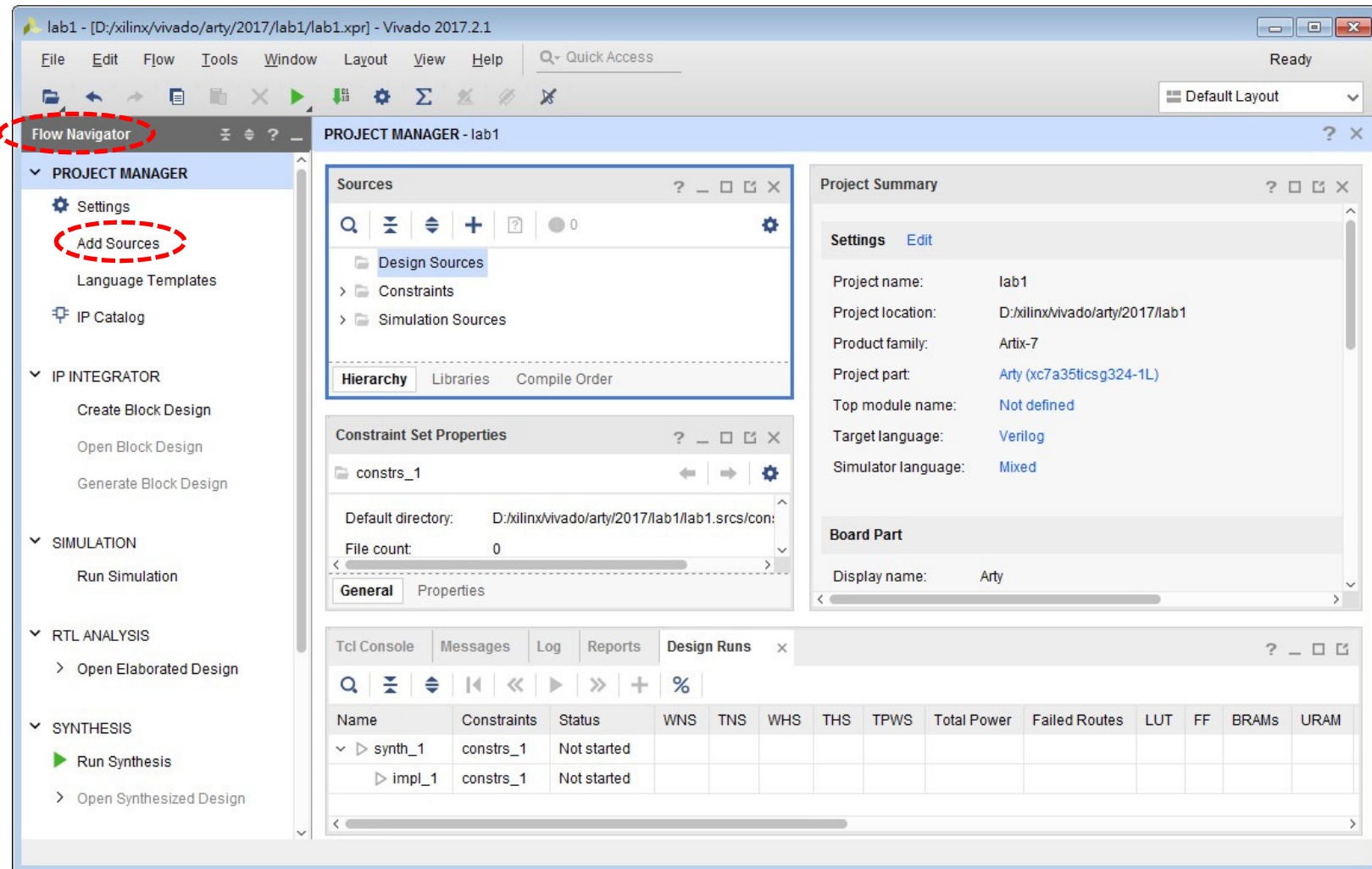


Specifying the Source Type to Create

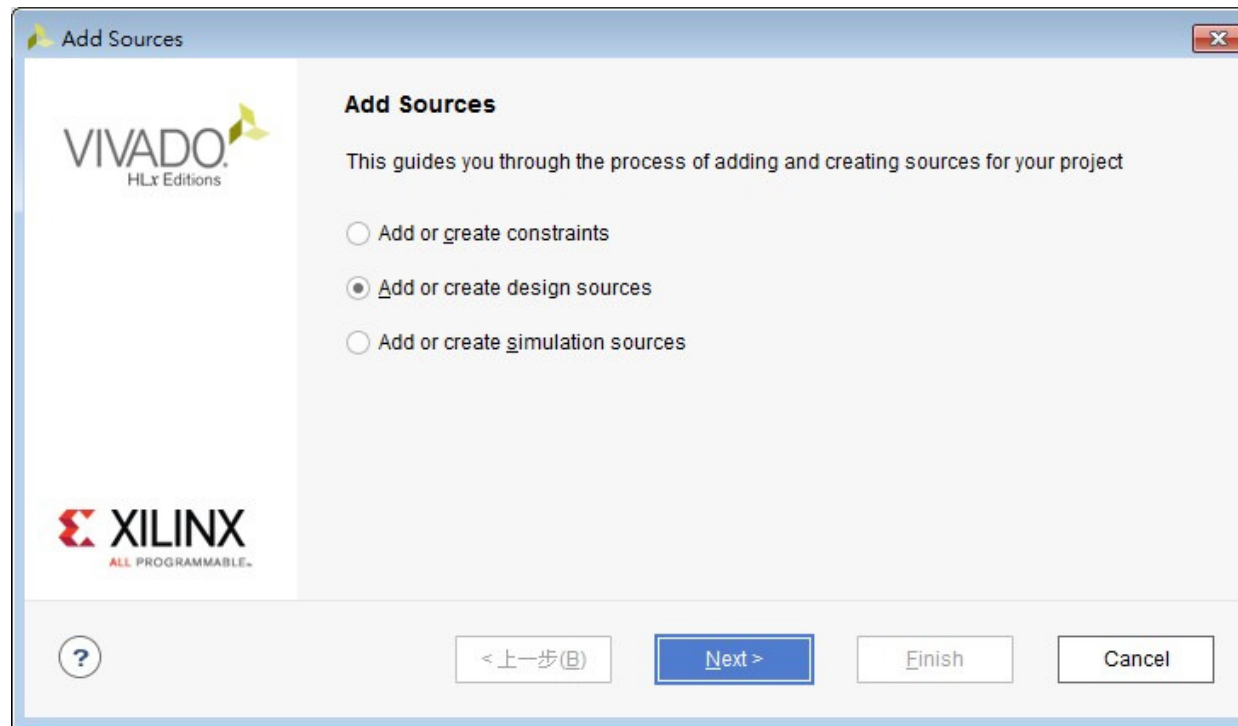- ❑ There are several types of source files in a circuit design project: design sources, constraint sources, simulation sources, and memory sources, etc.





Create a 4-bit Full Adder Design

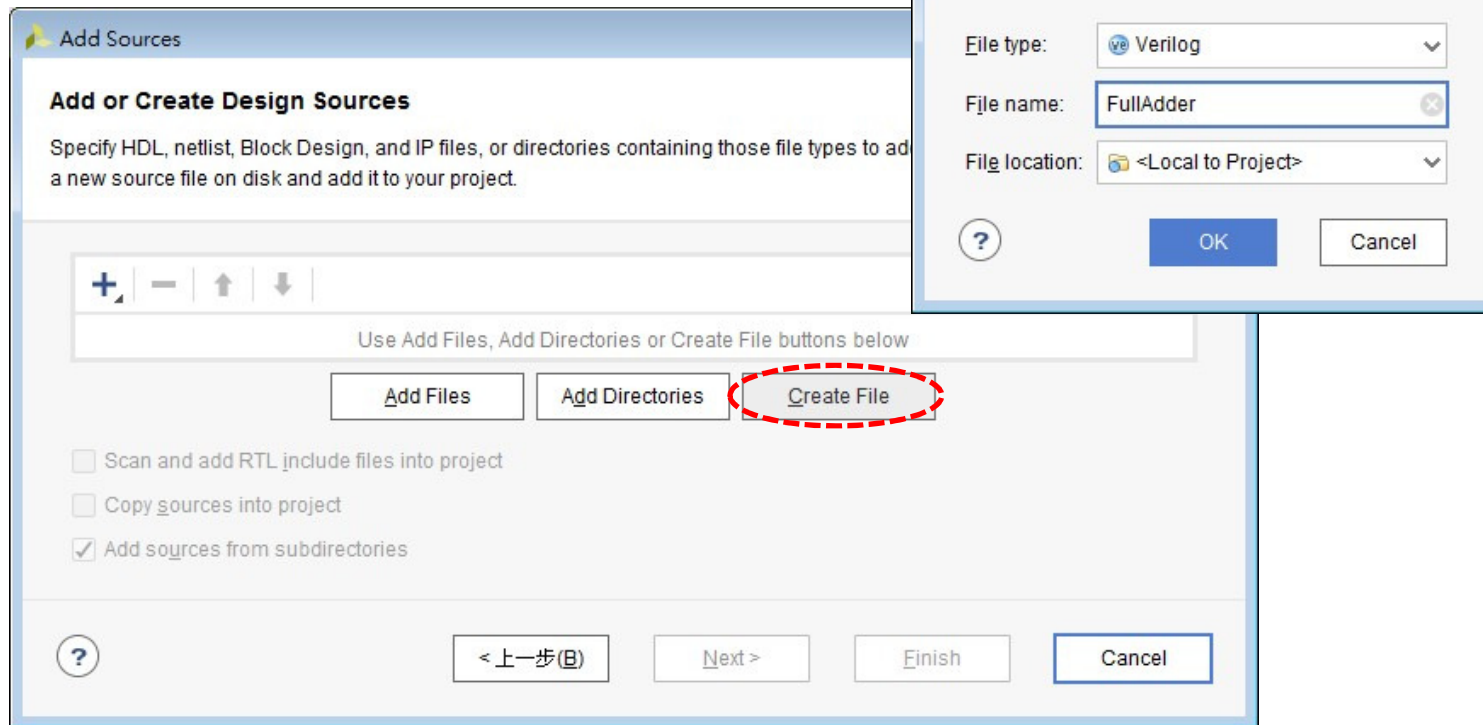- ❑ Let's create a design source from scratch!



Confirm to Create the Verilog Module

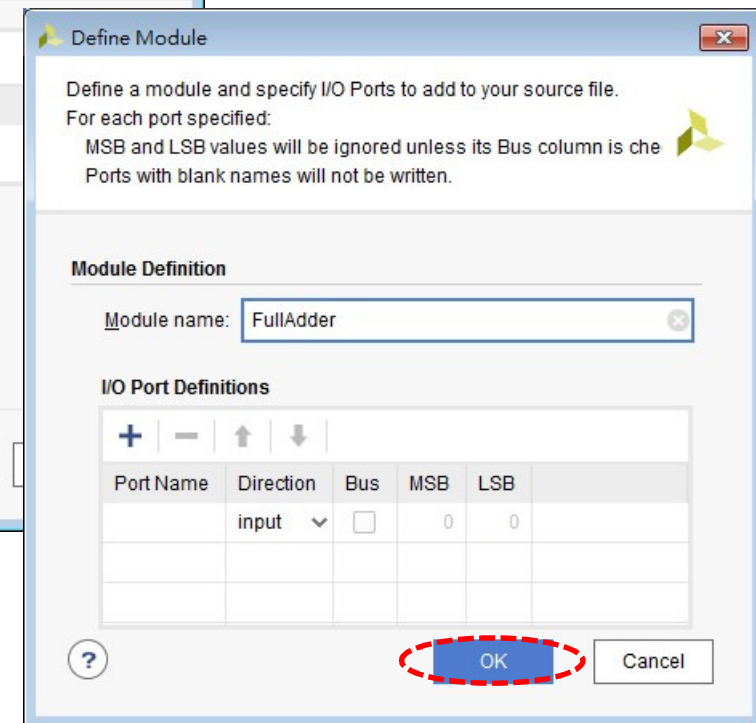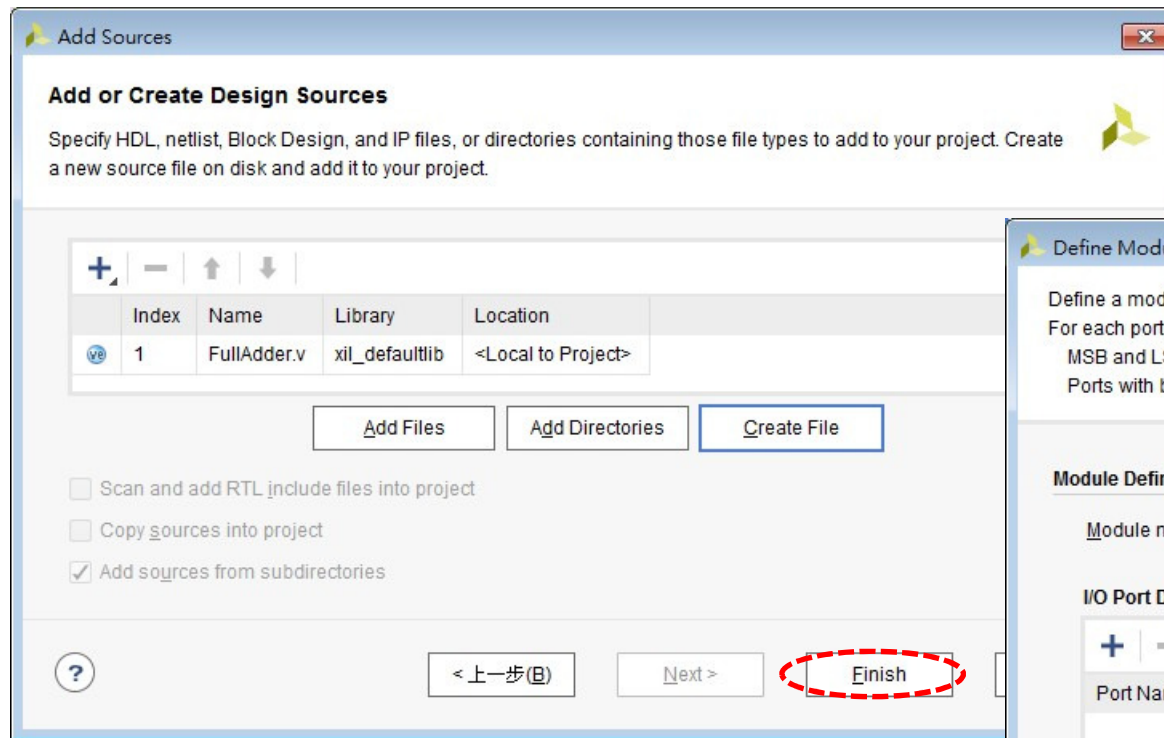- ❑ You can define your ports here or do it in the HDL code:



Type in the HDL Source Code

- ❑ You can now enter the following source code:

```
// ----- A four-bit full adder -----
module FullAdder(A, B, Cin, S, Cout);
    input [3:0] A, B;
    input Cin;
    output [3:0] S;
    output Cout;
    wire [2:0] t;


    FA_1bit FA0(.A(A[0]), .B(B[0]), .Cin(Cin), .S(S[0]), .Cout(t[0]));
    FA_1bit FA1(.A(A[1]), .B(B[1]), .Cin(t[0]), .S(S[1]), .Cout(t[1]));
    FA_1bit FA2(.A(A[2]), .B(B[2]), .Cin(t[1]), .S(S[2]), .Cout(t[2]));
    FA_1bit FA3(.A(A[3]), .B(B[3]), .Cin(t[2]), .S(S[3]), .Cout(Cout));
endmodule

// ----- A 1-bit full adder -----
module FA_1bit(A, B, Cin, S, Cout);
    input A, B, Cin;
    output S, Cout;

    assign S = Cin ^ A ^ B;
    assign Cout = (A & B) | (Cin & B) | (Cin & A);
endmodule
```


TestBench Design

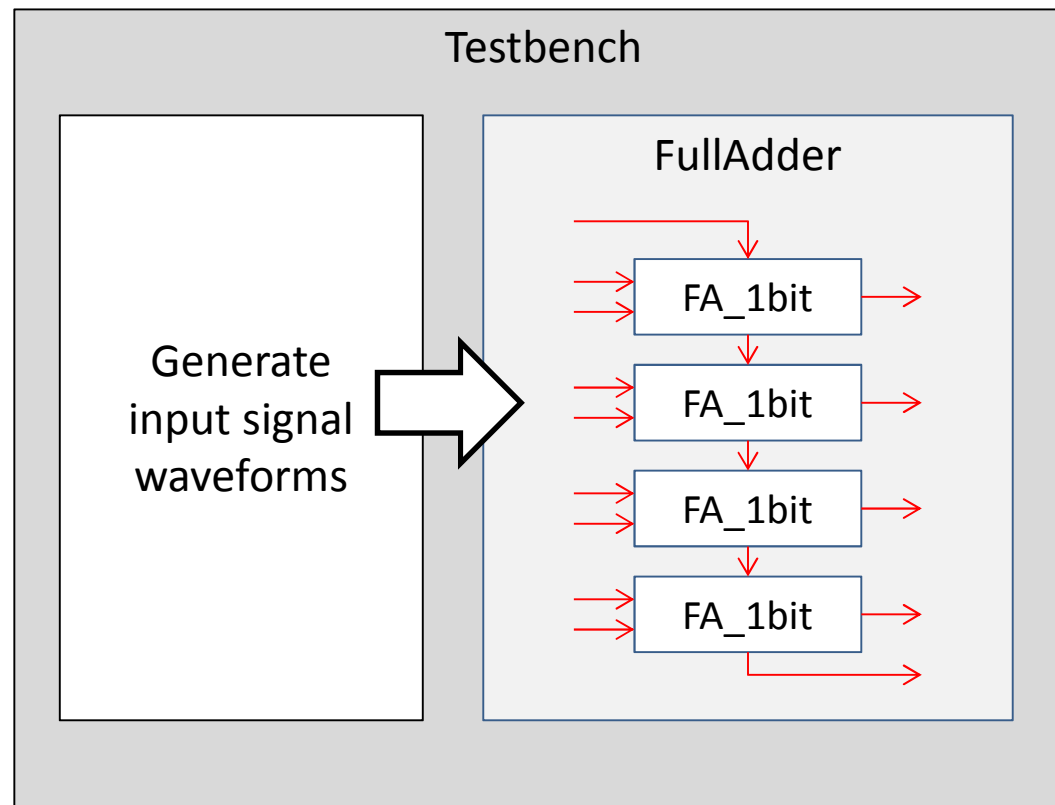- ❑ You must create a testbench to generate input signals that can feed into your circuit module, such that you can analyze the output to verify its correctness




Create the Testbench Source Code

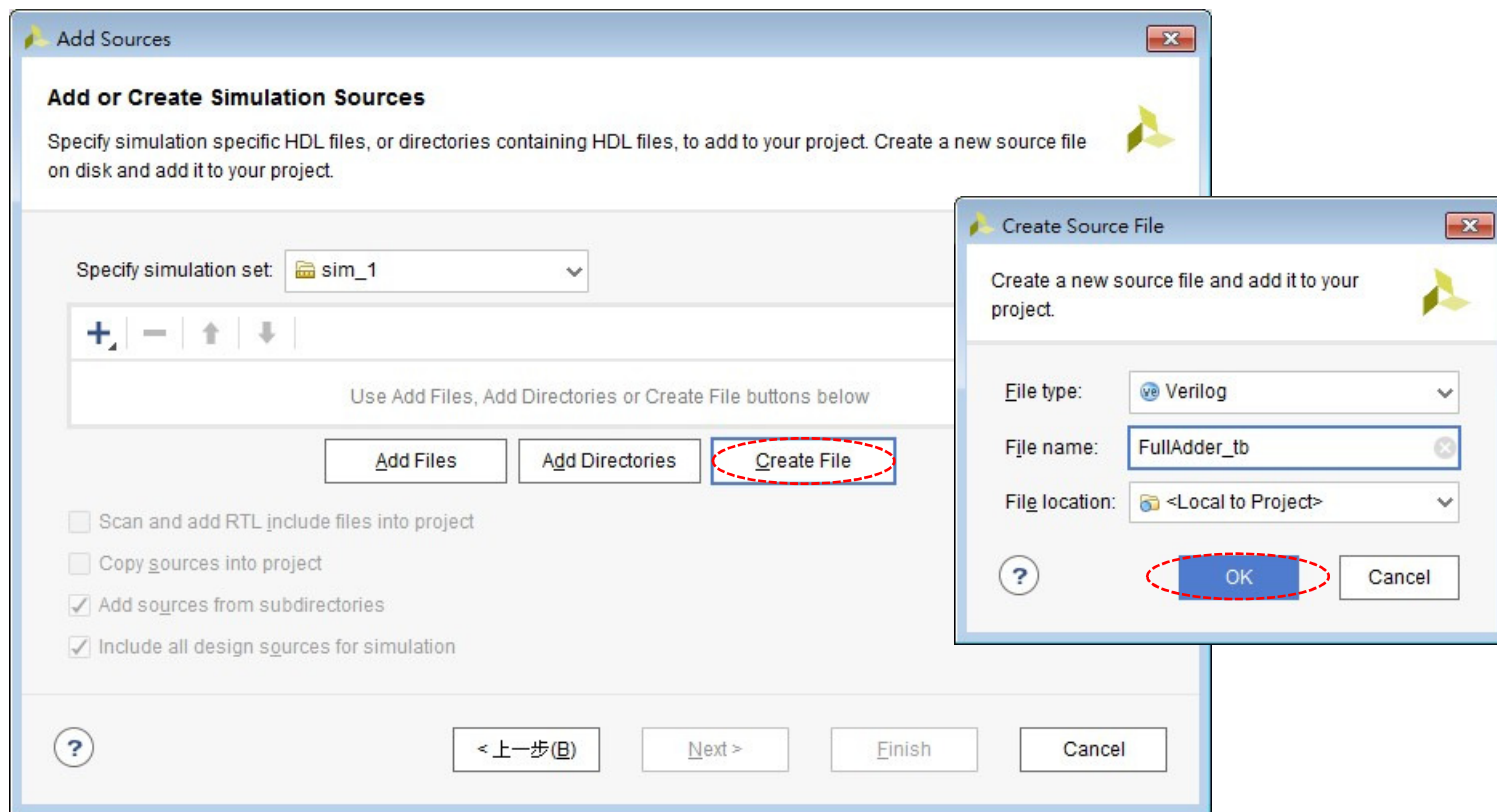- ❑ Click “Add Sources” button again, and this time, select “Add or create simulation sources”




Confirm the Creation of the Testbench

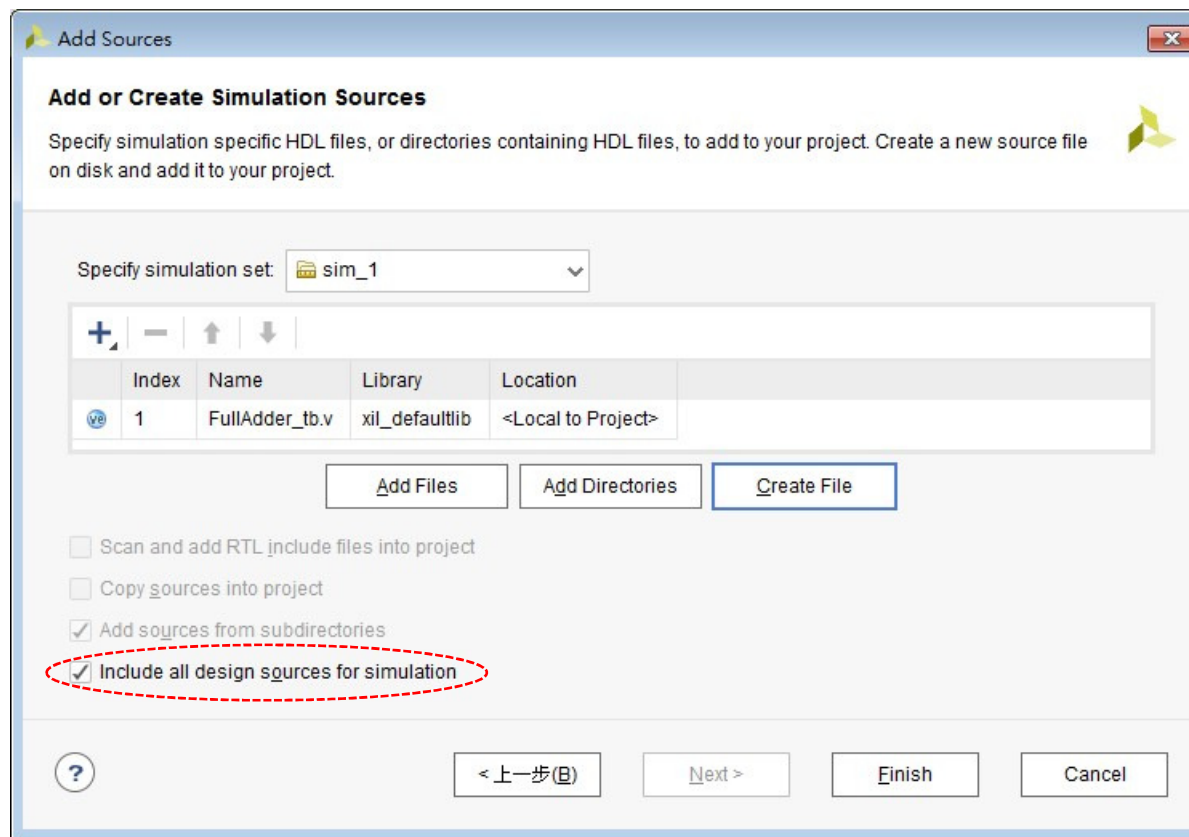- ❑ Here, we include the design sources into the simulation set so that we can test the modules under development




Create the Testbench Template

 - ❑ Hit “OK” then “Yes” to create an empty testbench template → top-level of the testbench template usually has no I/O ports



Type in the Testbench Source Code

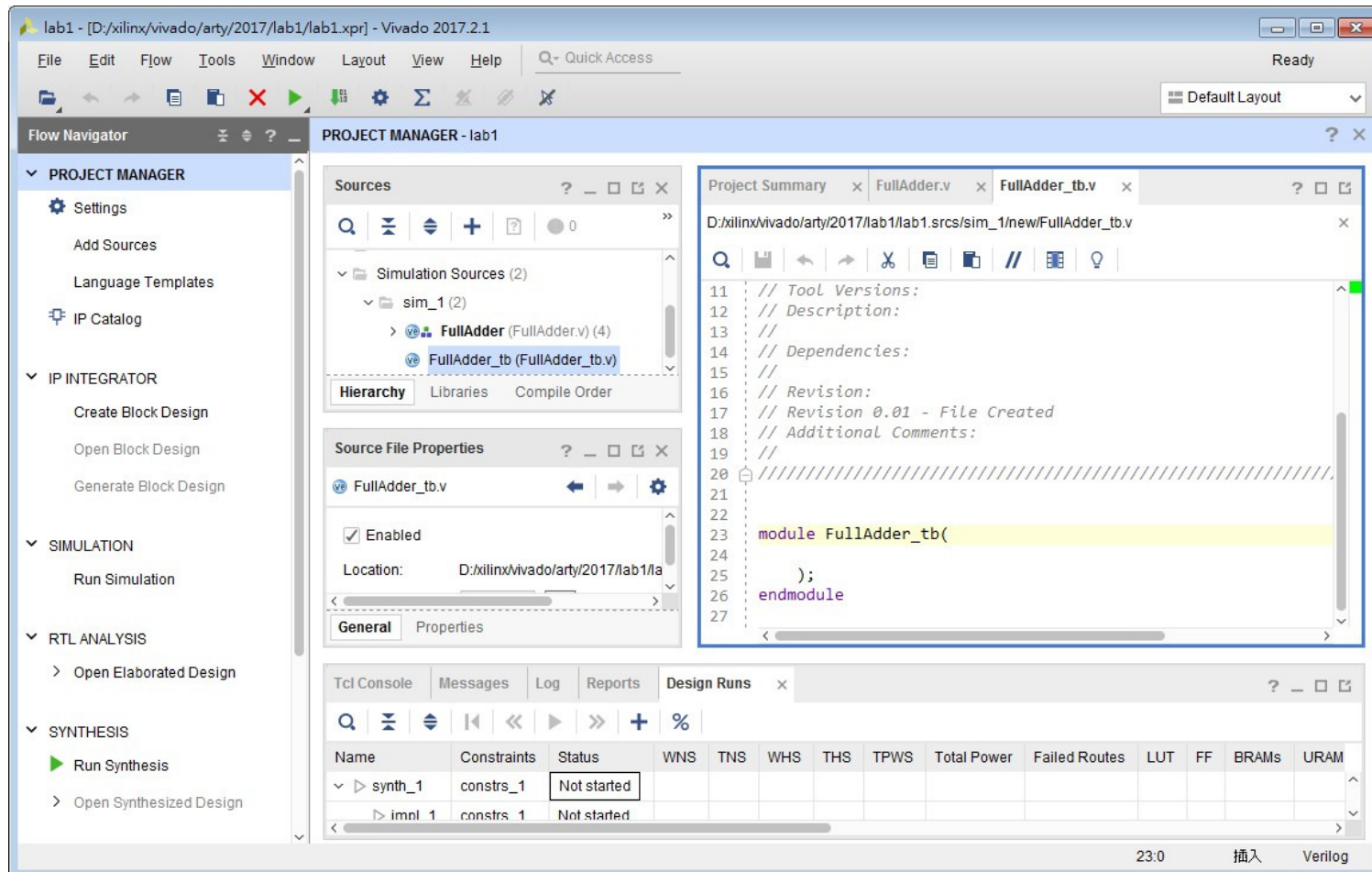- ❑ We can now type in (copy-paste) the testbench code:



The Sample Testbench Code

- ❑ The template created by Vivado is an empty module; we must add your own test pattern generator to it

```
module FullAdder_tb;

// inputs
reg clk = 1;
reg [3:0] A, B;
reg Cin;

// outputs
wire [3:0] S;
wire Cout;

// Instantiate the Unit
// Under Test (UUT)

FullAdder uut(
    .A(A),
    .B(B),
    .Cin(Cin),
    .S(S),
    .Cout(Cout)
);
```

```
// 100MHz clock generator
always
    #5 clk = !clk;


initial begin
    // Initialize Inputs
    A = 0; B = 0; Cin = 0;

    // Wait 100 ns for global
    // reset to finish
    #100;

    // Add stimulus here
    A = 4'b0101; B = 4'b1010;
    #50;
    A = 4'b1111; B = 4'b0001;
    #50;
    A = 4'b0000; B = 4'b1111;
    Cin = 1'b1;
    #50;
    A = 4'b0110; B = 4'b0001;
end
endmodule
```



Compile the Design for Simulation

❑ Now, you can run the simulation:

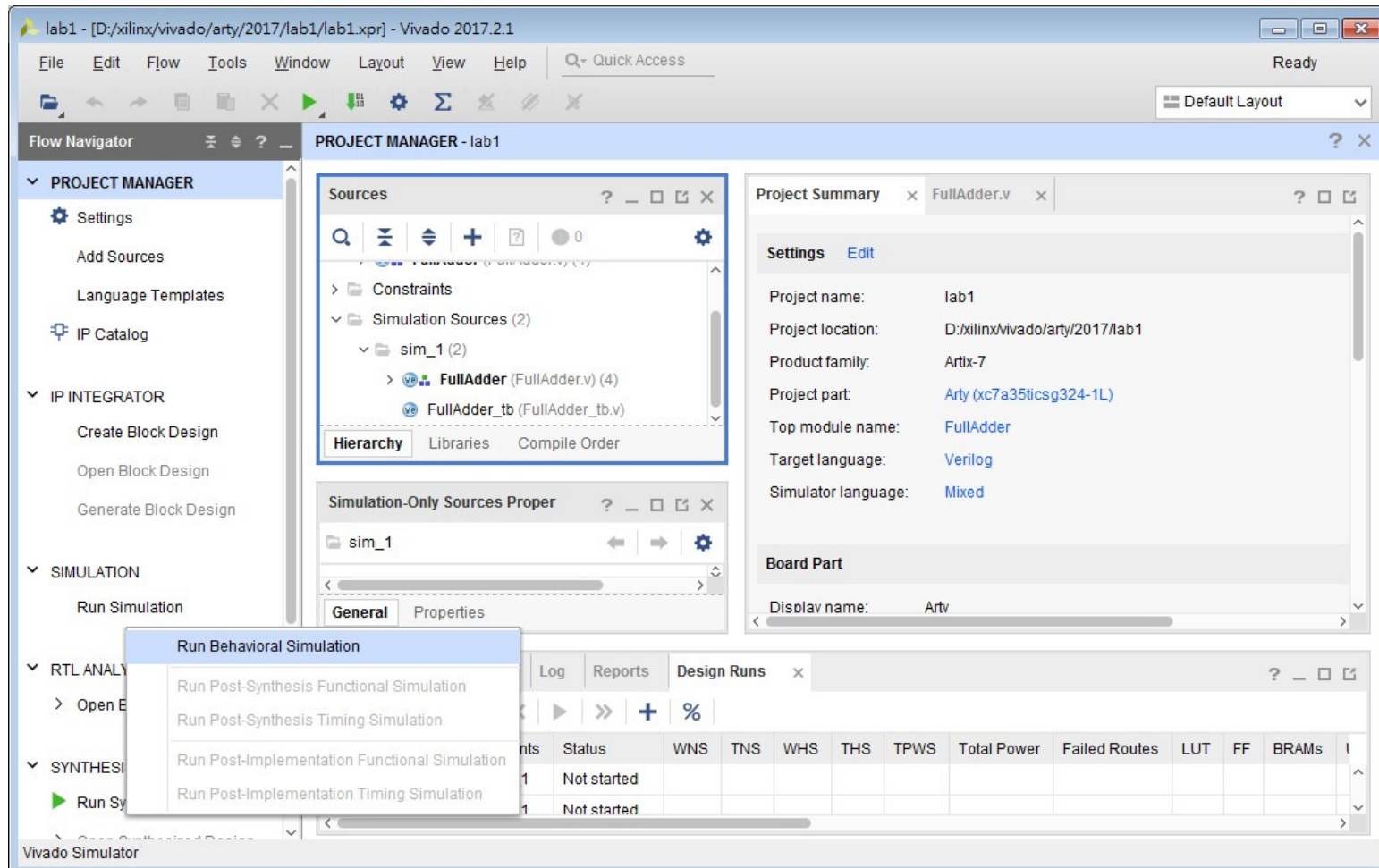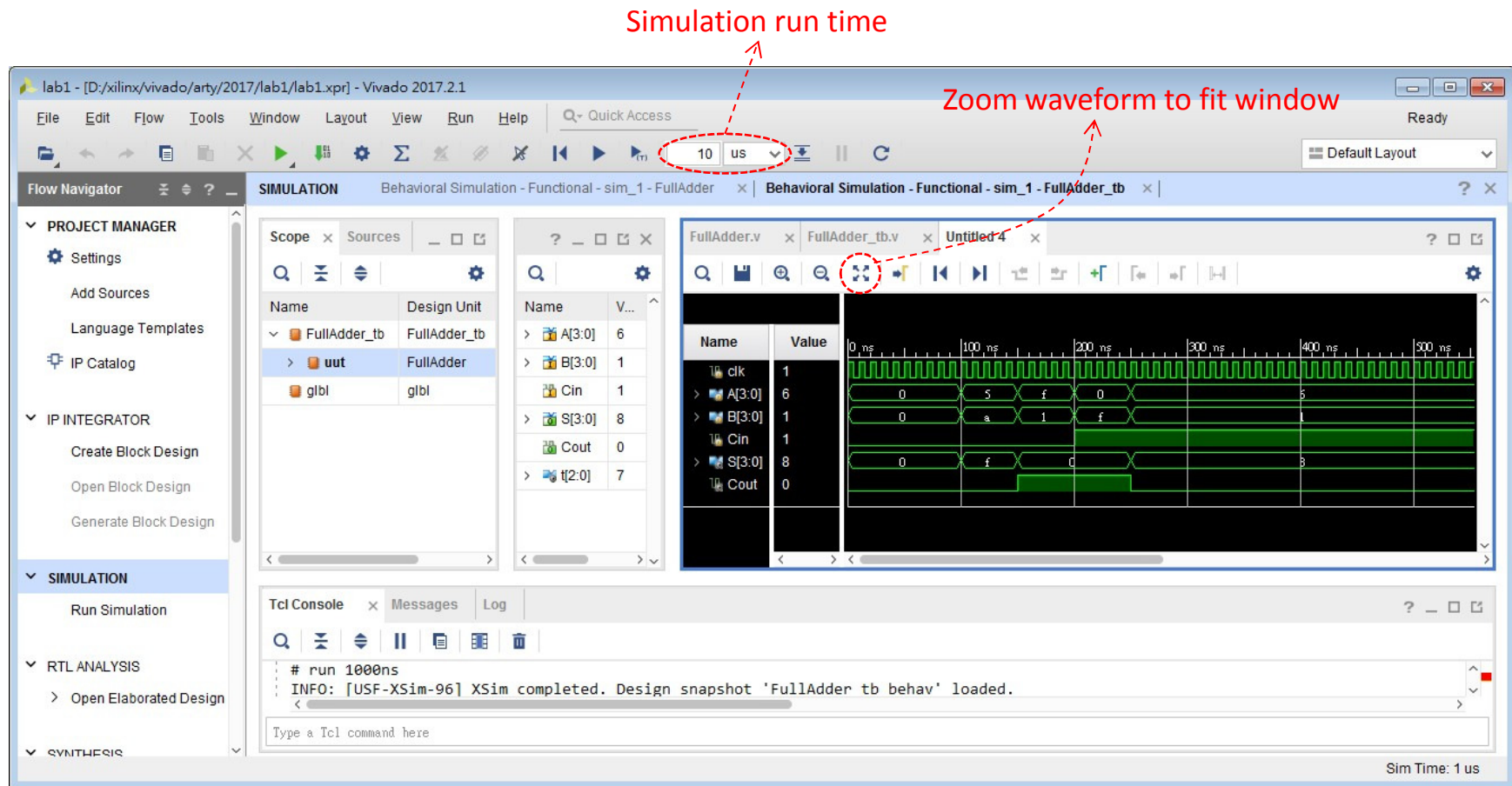

Vivado Simulator Window

- ❑ When the simulation is done, you get the waveforms:



Register Transfer-Level (RTL) Coding

- ❑ For our labs, you do not have to design the circuits purely at gate-level; you can write RTL codes
- ❑ For example, the four-bit adder module can be implemented using the RTL code simply as follows:

```
// ----- A four-bit full adder -----  
module FullAdder(A, B, Cin, S, Cout);  
    input [3:0] A, B;  
    input Cin;  
    output [3:0] S;  
    output Cout;  
  
    assign { Cout, S } = A + B + Cin;  
endmodule
```

Module Specification for Lab 1

- The input/output ports of the multiplier is as follows:

```
module SeqMultiplier(  
    input wire clk,  
    input wire enable,  
    input wire [7:0] A,  
    input wire [7:0] B,  
    output wire [15:0] C  
);
```

‘clk’ is the system clock,
‘enable’ activates the multiplication operation,
‘A’ is the 8-bit unsigned multiplicand input,
‘B’ is the 8-bit unsigned multiplier input, and
‘C’ is the 16-bit unsigned product output.

Sequential Binary Multiplier Behavior

- ❑ The behavior of sequential binary multiplication of 10111 and 10011 is as follows:

	00010111	→ multiplicand
×	00010011	→ multiplier
	00010111	
	00010111	
	00000000	
	00000000	
+	00010111	
	000110110101	→ product

- At each clock cycle, reads one bit from the multiplier and shift-and-adds the multiplicand to the product
- ❑ For digital circuit design, we can perform the process reversely

C Model of the Multiplier

- ❑ The C code that performs the sequential multiplication:

```
typedef unsigned char Byte;
typedef unsigned short Word;

SeqMultiplier(Byte A, Byte B, Word *C)
{
    int idx;


    *C = 0;
    for (idx = 8; idx != 0; idx--)
    {
        *C = *C << 1;
        if ((B & 0x80) == 0x80)
        {
            *C += A;
        }
        B = B << 1;
    }
}
```



Your task for lab1 is
to rewrite this C code
using Verilog!

 Example of Simulated Waveforms

- An example of the timing diagram of $239 \times 35 = 8365$



Stable output 8365 happens
8 cycles after enable == 1