

# Lab 9: Correlation Filter Design



National Chiao Tung University  
Chun-Jen Tsai  
12/8/2017

# Lab 9: Correlation Filter Circuit

- ❑ In this lab, you will design a correlation filter circuit and use it to detect the presence of a waveform
  - Your circuit has an SRAM that stores a 1-D waveform  $f[\cdot]$  of 1024 data samples and a 1-D pattern  $g[\cdot]$  of 64 data samples; each sample in  $f[\cdot]$  and  $g[\cdot]$  is an 8-bit **signed** number
  - When the user hit BTN0, your circuit will compute the cross-correlation function  $C_{fg}[\cdot]$  between  $f[\cdot]$  and  $g[\cdot]$ , and display the maximal value of  $C_{fg}[\cdot]$  and its position on the 1602 LCD
- ❑ The deadline of the lab is on 12/19

# What is a Correlation Filter

- ❑ Mathematically, a correlation filter is the sliding inner product between two signals  $f(x)$  and  $g(x)$ :

$$C_{fg}(x) = f(x) * g(x) = \int_{-\infty}^{\infty} f(s+x)g(s)ds$$

- If  $f(x)$  and  $g(x)$  are the same signal, it is called auto-correlation
  - If  $f(x)$  and  $g(x)$  are different signals, it is called cross-correlation
- ❑ Correlation filters can be used to find the period of a (noisy) periodic signal or the alignment of two aperiodic zero mean signals

# Digital Version of Correlation Filters

- A digital version of the correlation filter is:


$$c_{fg}[x] = f[x] * g[x] = \sum_{k=0}^{N-1} f[k+x]g[k]$$

- In this lab,  $f[0:1023]$  and  $g[0:63]$  are 8-bit signed arrays stored in an SRAM block, and the correlation function  $c_{fg}[0:959]$  has 960 elements


# Auto-Correlation Example

- The distances between the peaks of the auto-correlation function of a noisy periodic signals can be used to estimate the period of the signal:

a signal  $f(x)$

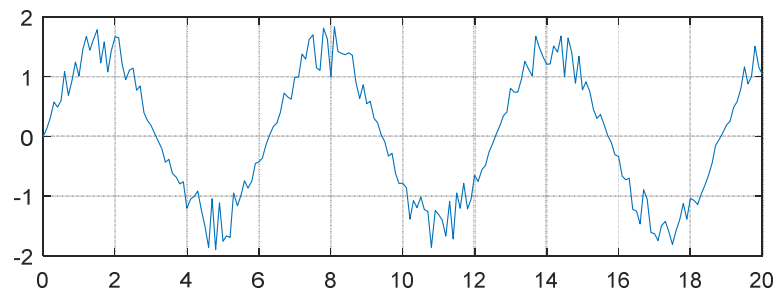


autocorrelation  $C_{ff}(y)$

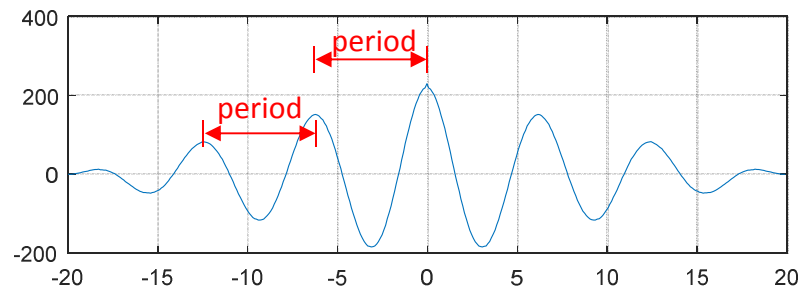
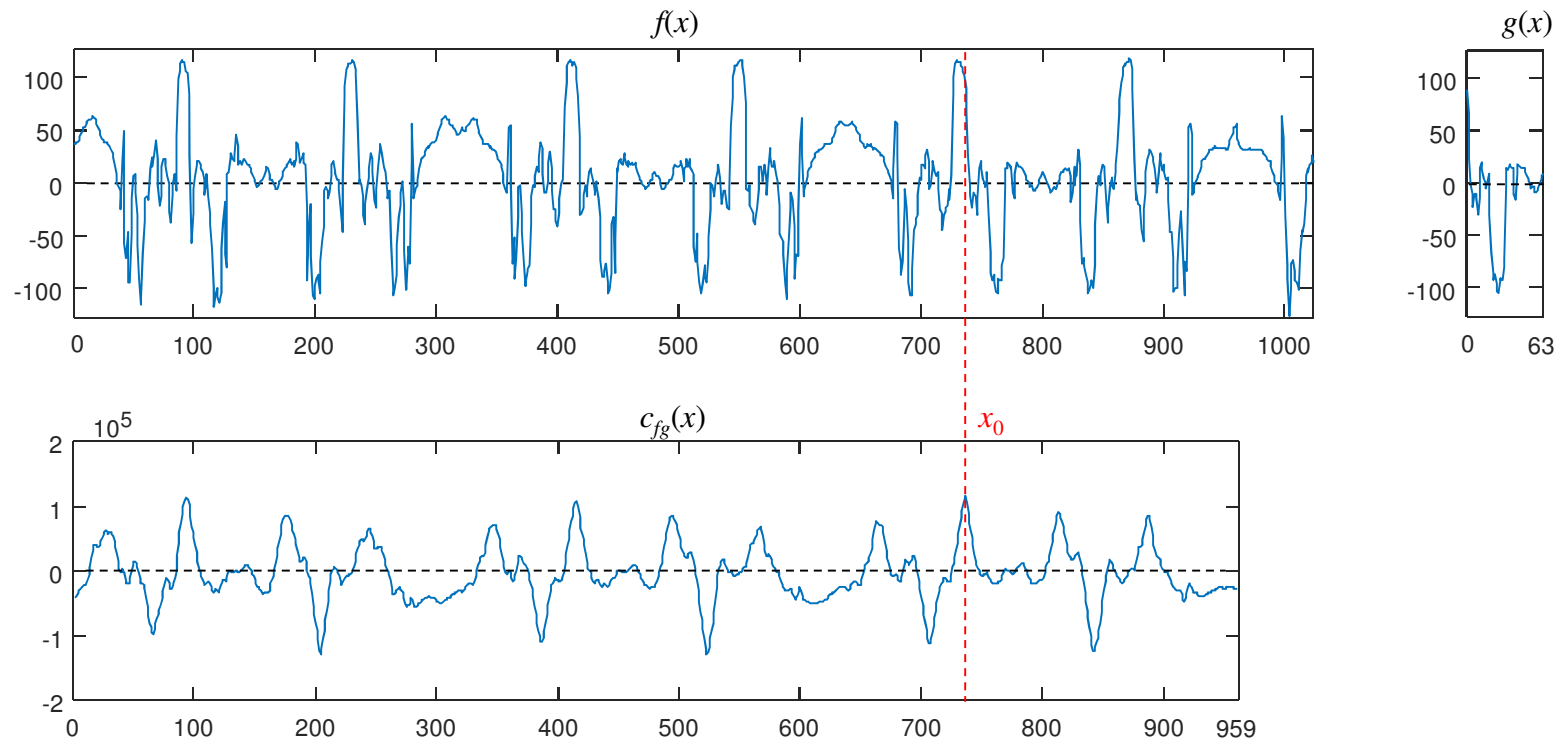
# Cross-Correlation Example

- The maximal location  $x_0$  of the cross-correlation function between  $g(x)$  and  $f(x)$  means that a signal most similar to  $g(x)$  is located at  $x_0$  of  $f(x)$ †:



† Note that  $f(x)$  and  $g(x)$  have near zero means and  $g(x)$  should not be too short.

# The C Model of Correlation


- A short C-model that computes the correlation function between  $f[]$  and  $g[]$  and record the maximal  $c_{fg}[]$  and its location is as follows:

```
char f[1024] = { ... };
char g[64] = { ... };
int c[960];
int x, y, k, sum, max, max_pos;

max = max_pos = 0;
for (x = 0; x < 1024 - 64; x++)
{
    sum = 0;
    for (k = 0; k < 64; k++)
    {
        sum += f[k+x] * g[k];
    }
    c[x] = sum;
    if (sum > max) max = sum, max_pos = x;
}
```
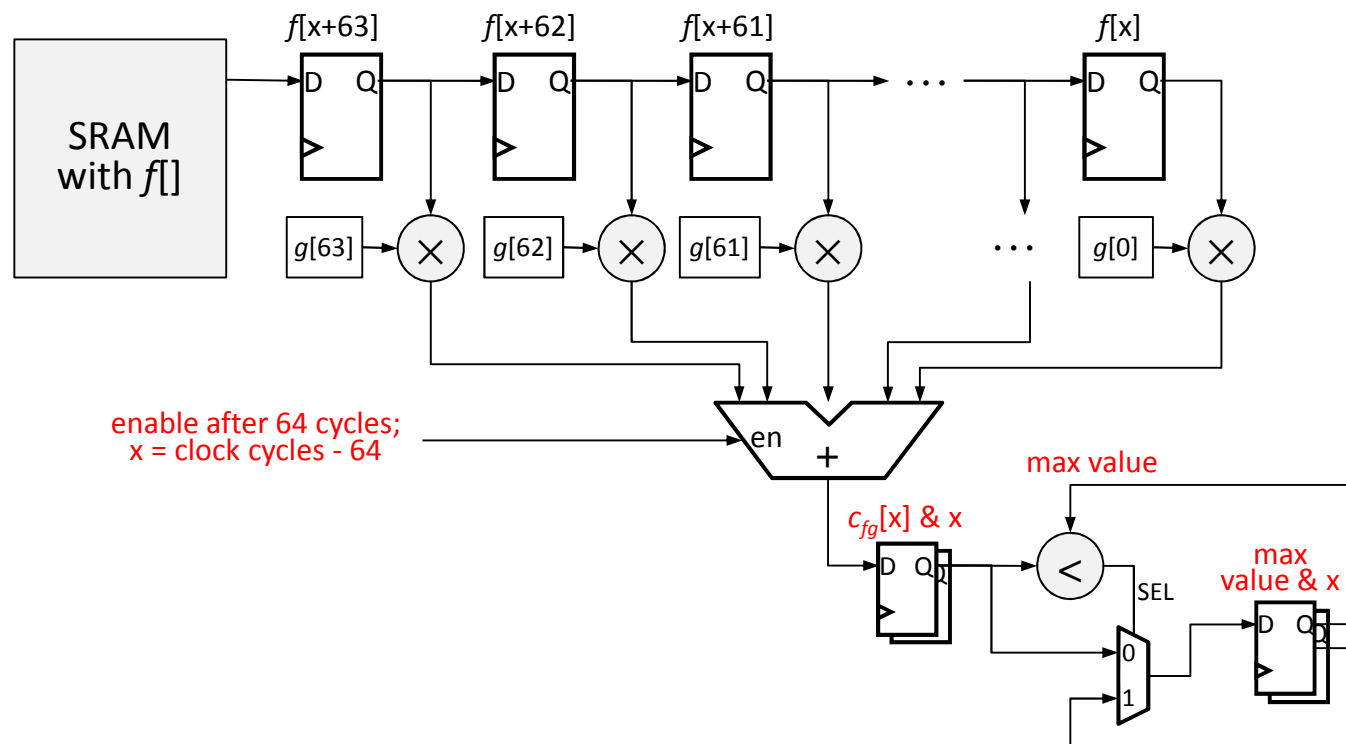
# Correlation Circuit Design

- ❑ You can use a chain of shift registers to read data from the SRAM, begin at address 0 and ends at 1023
  - The output  $c_{fg}[]$  should be a signed register of at least 22 bits.





# The Sample Code of Lab 9 (1/3)

- ❑ The sample code of lab 9 shows you how to create a SRAM block in FPGA with some data pre-stored in it
  - The signal data we use for  $f[]$  and  $g[]$  are pre-stored in SRAM  
→ need a 2KB SRAM
  - Initialization of a SRAM can be done as follows:

```
// This is a code segment from the sram module.  
  
// Declaration of the memory cells  
reg [DATA_WIDTH-1 : 0] RAM [RAM_SIZE - 1:0];  
  
// -----  
// SRAM cell initialization  
// -----  
initial begin  
    $readmemh("signals.mem", RAM);  
end
```


```
24  
24  
27  
26  
29  
2c  
2f  
32  
...
```

This is "signals.mem"

→ \$readmemh() is only synthesizable for FPGAs
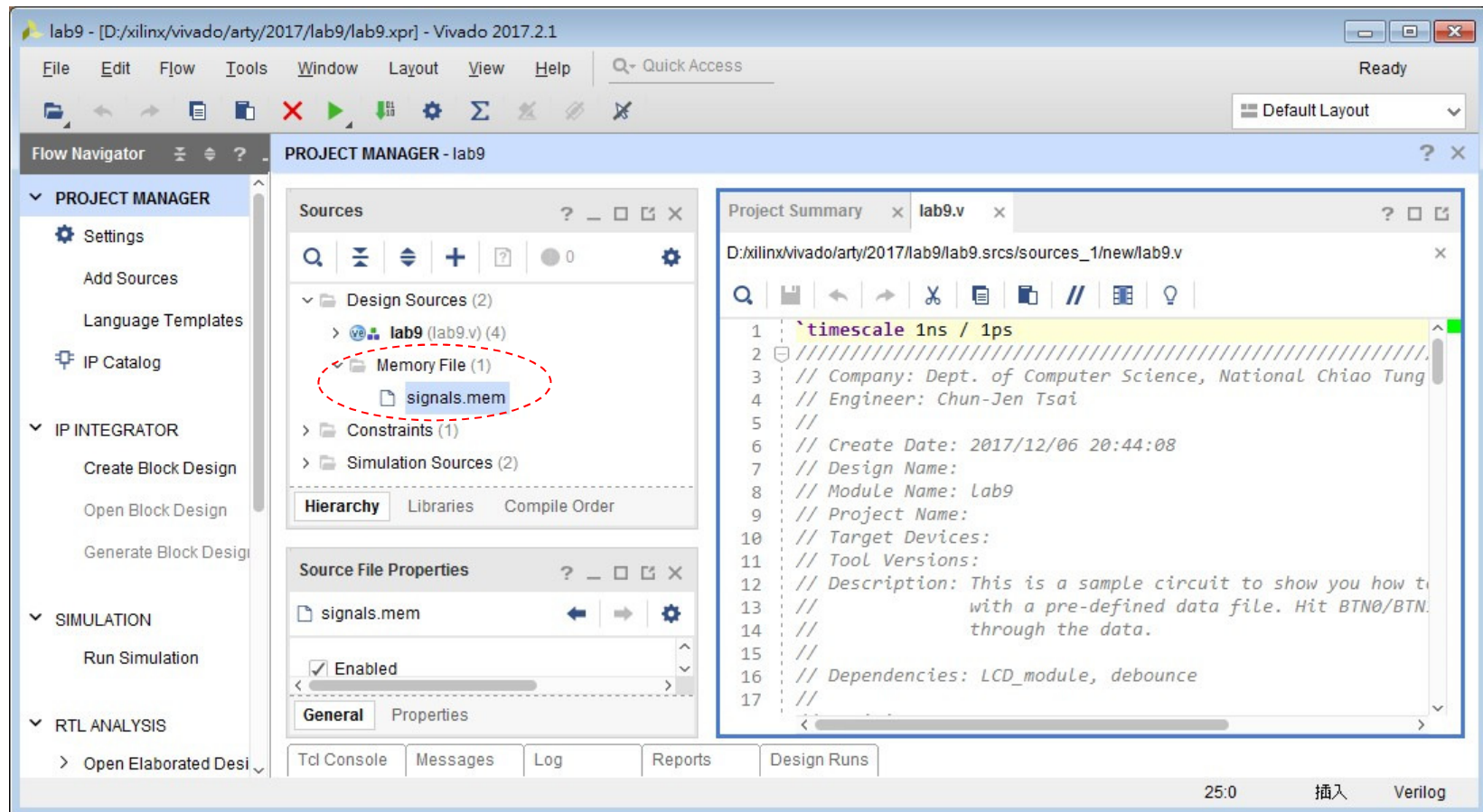
# The Sample Code of Lab 9 (2/3)

- ❑ The memory data file, signals.mem, is added into the Vivado project space as a design source file:



# The Sample Code of Lab 9 (3/3)

- ❑ After configuring the circuit into the FPGA, you will see the following 1602 LCD screen:

```
Sample at [000h]  
is equal to +24h
```

- ❑ You can use BTN0 and BTN1 to browse through all the data of  $f[]$  and  $g[]$  in SRAM
  - The array  $f[]$  is stored in SRAM address 0 ~ 1023, while the array  $g[]$  is stored in 1024 ~ 1087

# What You have to Do in Lab9

- ❑ In Lab 9, after you configured the FPGA, the 1602 LCD should show the following screen:

```
Press BTN0 to do  
x-correlation...
```

If the user presses BTN0, the correlation circuit should be activated. When the circuit is done, the maximal value of the correlation and its location should be displayed on the LCD:

```
Max value 01C44D  
Max location 2E0
```